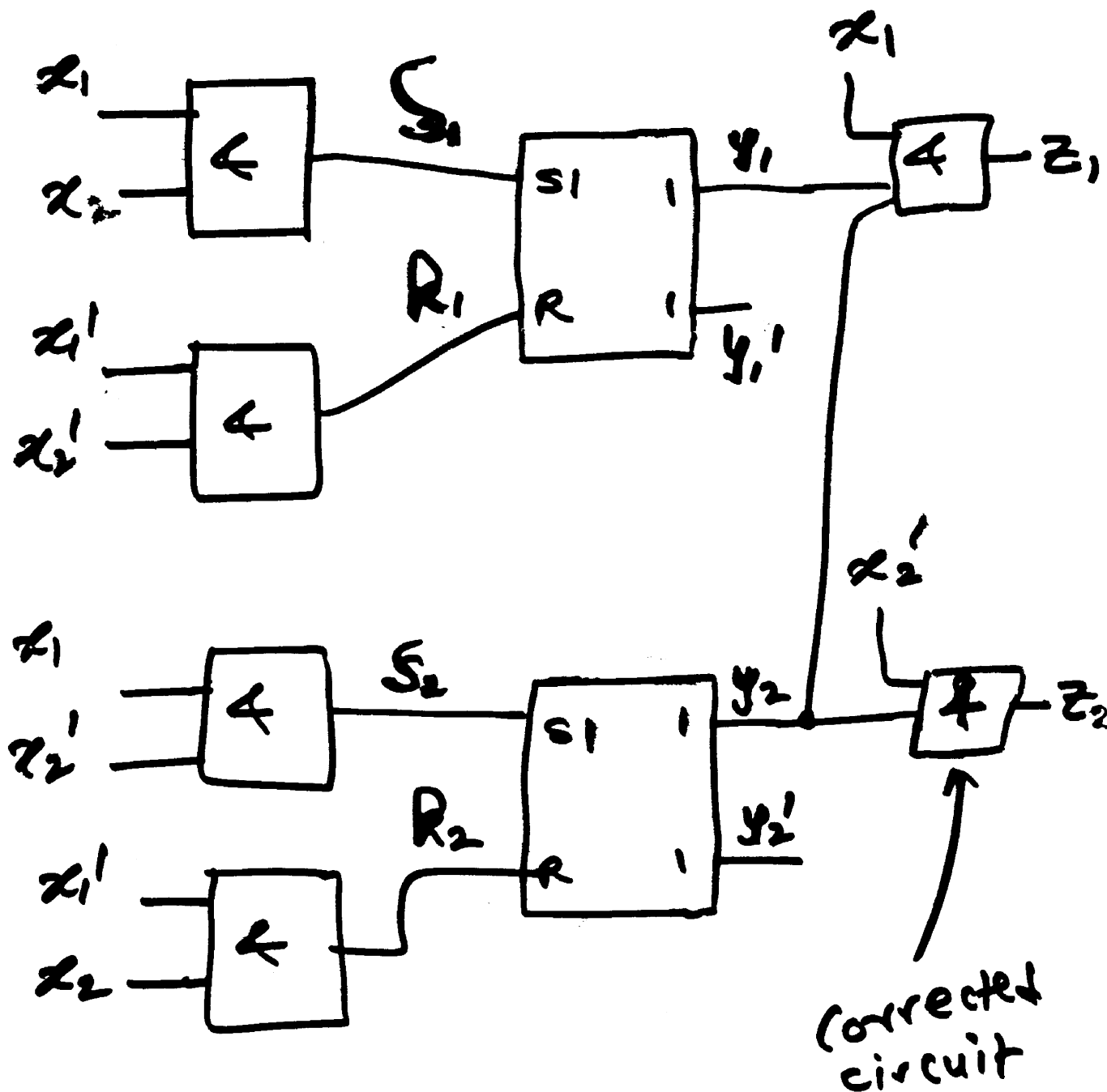


Analysis of sequential circuits with latches



Excitation table + characteristic function \Rightarrow transition table

stable states

x_1	x_2	y_1	y_2	Y_1	Y_2	z_1	z_2
0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	1
0	0	1	0	0	1	0	1
0	0	1	0	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	0	0	0
0	1	1	0	1	0	0	0
1	1	1	1	1	1	1	0
1	1	1	0	1	0	0	0
1	0	0	0	0	1	0	0
1	0	0	1	0	1	0	1
1	0	1	0	1	1	1	1

stable state (13)

The table on previous slide can be presented differently to obtain the so-called transition table ~~table~~ shown below, and output table shown later

$y_1 y_2 \backslash x_1 x_2$	00	01	11	10
00	00	00	10	01
01	01	00	11	01
11	01	10	11	11
10	00	10	10	11
	y_1	y_2		

← transition table

$y_1 y_2 \backslash x_1 x_2$	00	01	11	10
00	00	00	00	00
01	01	00	00	01
11	01	00	10	11
10	00	00	00	00
	x_1	x_2		

← output table
 $z_1 z_2$

(13A)

A total state

$$x_1, x_2, y_1, y_2$$

is stable if in this state

$$Y_1, Y_2 = y_1, y_2$$

otherwise, the total state is unstable.

In the transition table, if we replace ~~the~~ binary "code" for each state by a letter or name of some sort, the resulting table is called a state table.

internal state
S

	x_1, x_2			
	00	01	11	10
A	(A)	(A)	D	B
B	(B)	A	C	(B)
C	B	D	(C)	(C)
D	A	(D)	(D)	C

state S

A: 00
B: 01
C: 11
D: 10

The transition table shows the "next" state \Rightarrow When the total state is not stable, the circuit will not stay in the "next" state for long, and will make another transition. These transitions will continue until a stable state is reached.

A "flow table" shows, for each total state, the final stable state that will be reached.

see next
slide

Transition table:


$y_1 y_2$ \ $x_1 x_2$	00	01	11	10
00	00	00	10	01
01	01	00	11	01
11	01	10	11	11
10	00	10	10	11

Flow table:

$y_1 y_2$ \ $x_1 x_2$	00	01	11	10
00	00	00	10	01
01	01	00	11	01
11			11	11
10		10	10	

For this example, transition table and flow table happen to be identical.

Another Example :

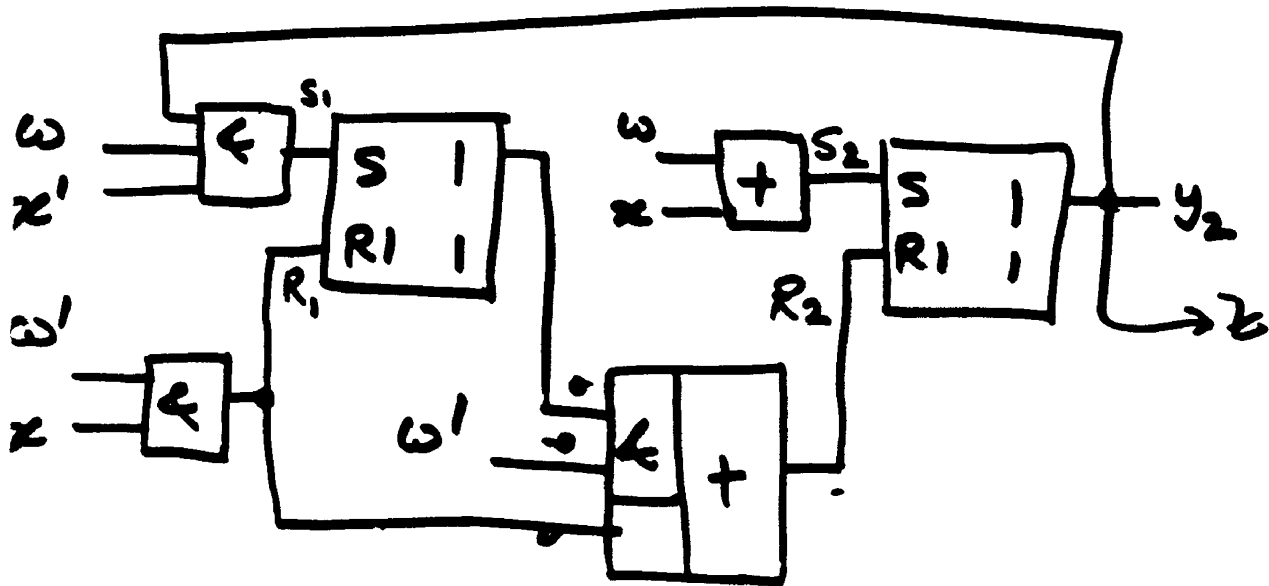

Excitation functions : $\begin{cases} S_1 = y_2 \omega x' \\ R_1 = \omega' x \\ S_2 = \omega + x \\ R_2 = y_1 \omega' + R_1 = \omega' (x + y_1) \end{cases}$


Next state functions
obtained using the characteristic function
 $Y = R'(s + y)$

$$Y_1 = R'_1 (s_1 + y_1) = \frac{\omega x' y_2 + x' y_1 + \omega y_1}{s_1 + y_1}$$

$$Y_2 = R'_2 (s_2 + y_2) = \frac{\omega + x' y_1 y_2}{s_2 + y_2}$$

Transition table

w,x	y_1, y_2	00	01	11	10
00		00	00	01	01
01		01	00	01	11
11		10	00*	11	11
10		10	00	11	11
			y_1, y_2		

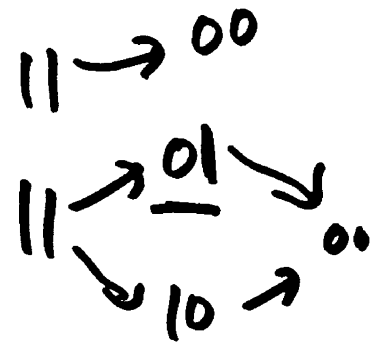

* denotes a race



both y_1 & y_2 change together

$w,x = 01$

$11 \rightarrow 01 \rightarrow 00$

$11 \rightarrow 10 \rightarrow 00$

A race is a critical race if the order in which y_1 and y_2 change affects the final state.

Otherwise, it is not a critical race.

Analysis of Sequential Circuits with Feedback Loops


Break feedback loops with inserting hypothetical amplifiers



Characteristic function of



$$Y = E$$

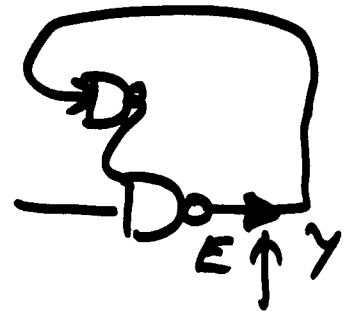

Excitation functions: $y_1 = x_1 x_2 + y_1 (x_1 + x_2)$

$y_2 = x_1 x_2' + y_2 (x_1 + x_2')$

Next state functions $y_1 = E_1$, $y_2 = E_2$

Transition Table
 can be obtained using above
 equations.

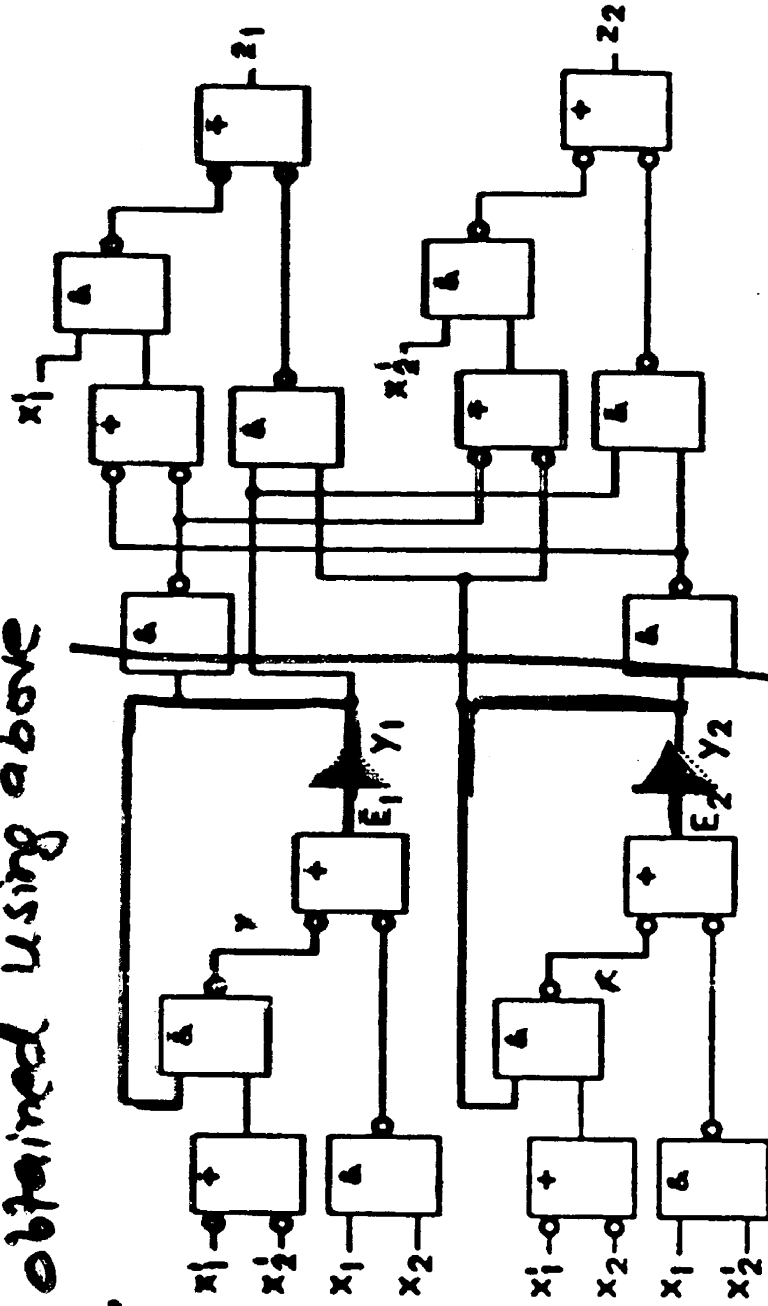


Figure 7.5-5 Sequential circuit constructed of NAND gates.

		x_1, x_2			
		00	01	11	10
y_1, y_2	00	00	00	10	01
	01	01	00	11	01
	11	01	10	11	11
	10	00	10	10	11
		y_1, y_2			

← Transition Table
 (Since $E=y$, excitation table is identical to transition table)

Outputs: write equations from the circuit:

$z_1 =$

$z_2 =$

Exercise

Obtain output table using these equations

Transition table. x_1, x_2

		x_1, x_2			
		00	01	11	10
y_1, y_2	00	00	00	10	01
	01	01	00	11	01
	11	01	10	11	11
	10	00	10	10	11



State table


		x_1, x_2			
		00	01	11	10
S	1	1	1	4	2
	2	2	1	3	2
	3	2	4	3	3
	4	1	4	4	3

- 00 \Rightarrow 1
- 01 \Rightarrow 2
- 11 \Rightarrow 3
- 10 \Rightarrow 4

⊙ denote stable state

S

22

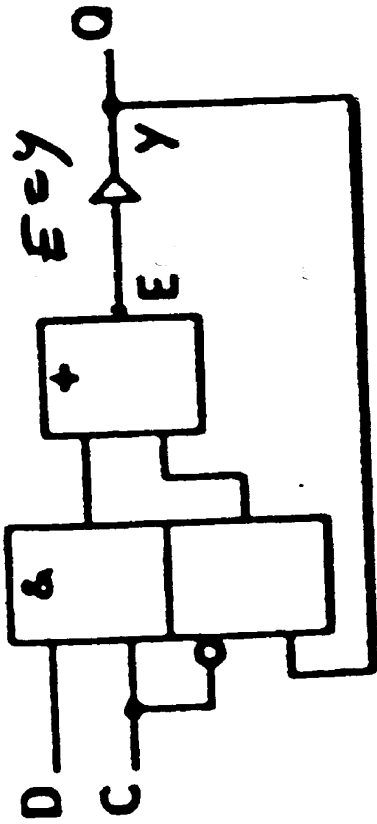

$$E = Y = DC + C'Y$$

(a)

Y	0	1	Y
0	0	0	0
1	1	1	1

CD
00 01 11 10 0

(b)

Figure 7.5-6 D latch analysis: (a) latch circuit; (b) transition table.

$$E = DC + C'Y$$


excitation function

$$Y = E$$

(characteristic)

next state function

23

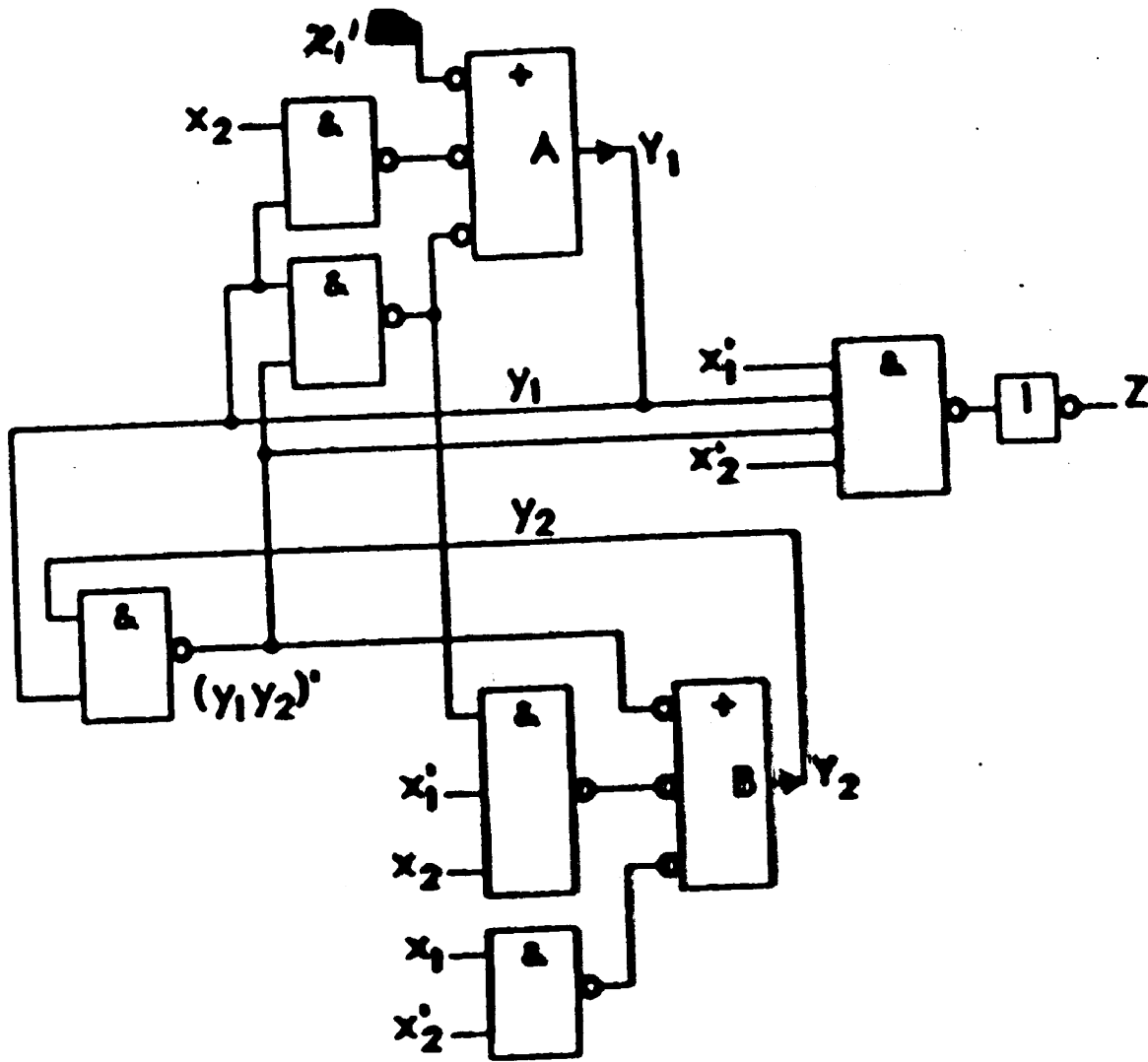

$$\begin{aligned}
 Y_1 &= x_1' + x_2 y_1 + y_1 (y_1 y_2)' = x_1' + x_2 y_1 + y_1 y_2' \\
 Y_2 &= y_1 y_2 + (y_1' + y_1 y_2) x_1' x_2 + x_1 x_2' = y_1 y_2 + x_1' x_2 y_1 + x_1 x_2' \\
 Z &= x_1' x_2' y_1 (y_1' + y_2') = x_1' x_2' y_1 y_2'
 \end{aligned}$$

Figure 7.6-1 Sequential circuit illustrating races.

Excitation table and transition table identical because $\gamma = E$.

		$x_1 x_2$			
		00	01	11	10
$y_1 y_2$	00	00	01	10	11
	01	00	01	10*	11
	11	01	11	11	11
	10	10	10	10	11

* denotes a race