
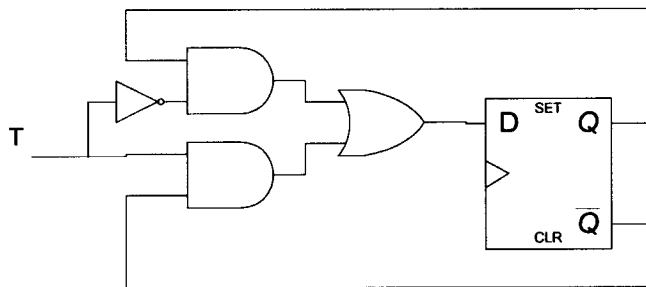
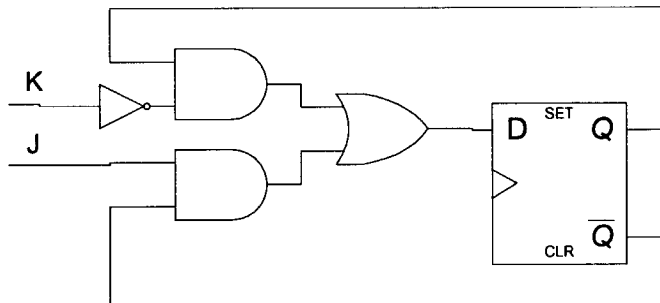


# ECE 462 Homework #10 Solutions (Spring 2005)

A)

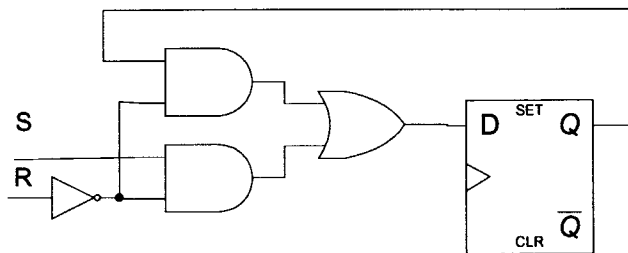

**C** / 8.2b (2 pts)

Excitation equations:

$$Q_1^+ = D \langle \text{CLOCK} \rangle \uparrow = ((X' + Q_1'')Q_2')' \langle \text{CLOCK} \rangle \uparrow = (XQ_1' + Q_2) \langle \text{CLOCK} \rangle \uparrow$$

$$\begin{aligned} Q_2^+ &= (J'K'Q_2 + JK' + JKQ_2') \langle \text{CLOCK} \rangle \uparrow \\ &= (X'(Q_1'X + Q_1X')'Q_2 + X(Q_1' + Q_1X')' + X(Q_1'X + Q_1X')Q_2') \langle \text{CLOCK} \rangle \uparrow \\ &= (X'Q_1'Q_2 + XQ_1 + XQ_2') \langle \text{CLOCK} \rangle \uparrow \end{aligned}$$

$$J = X$$

$$K = Q_1 \oplus X = Q_1'X + Q_1X'$$

$$Z = (Q_1Q_2)' = Q_1' + Q_2$$

Transition table:


		<CLOCK>↑				
Q1	Q2	0		1		Z
0	0	0	0	1	1	1
0	1	1	1	1	0	1
1	0	1	0	1	1	1
1	1	0	0	0	1	0

Q1+Q2+

State/Output table:

		<CLOCK>↑				
Q1	Q2	s	0	1	Z	
0	0	A	A	C	1	
0	1	B	C	D	1	
1	0	C	D	C	1	
1	1	D	A	B	0	


State/Output diagram:

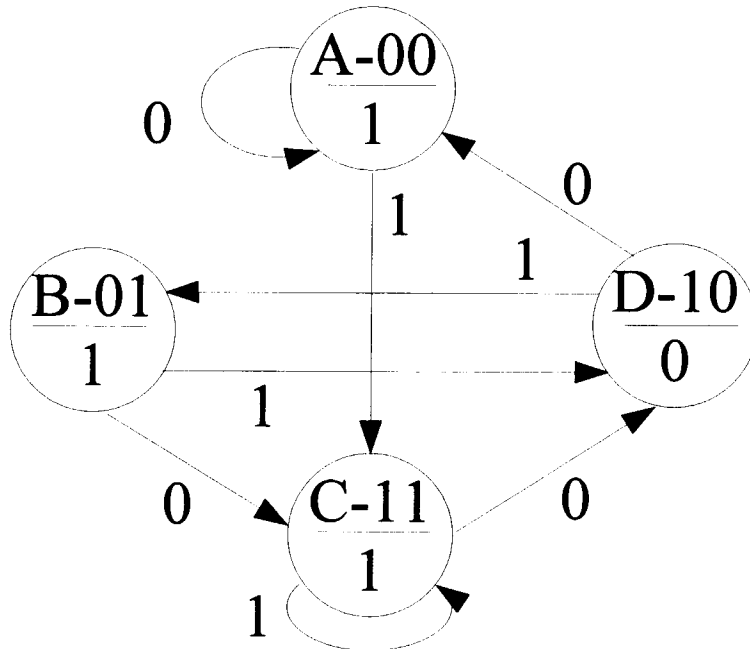

D)



	00	01	11	10
1	1	-	7	4
2	2	3	8	-
3	6	-	2	3
4	6	6	1	-
5	-	A	-	4
6	2	6	8	4
7	8	4	B	-
8	7	3	5	2

a) A = -    B = -

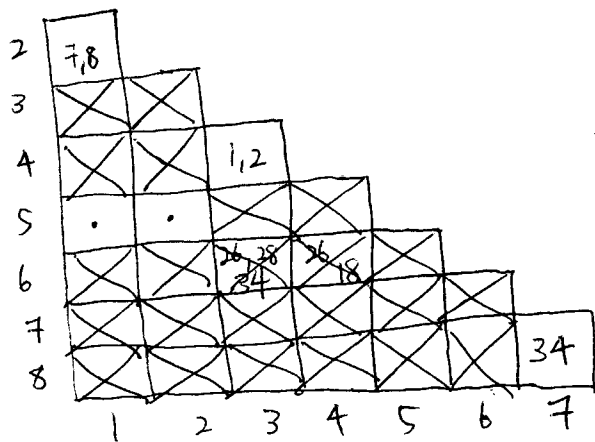

	00	01	11	10	$z_1 z_2$
$[1,2,5] = A$	(A)	B	C	B	00
$[3,4] = B$	D	D	A	(B)	01
$[7,8] = C$	(C)	B	A	A	10
$[6] = D$	A	(D)	C	B	01

b) A = 6    B = -

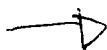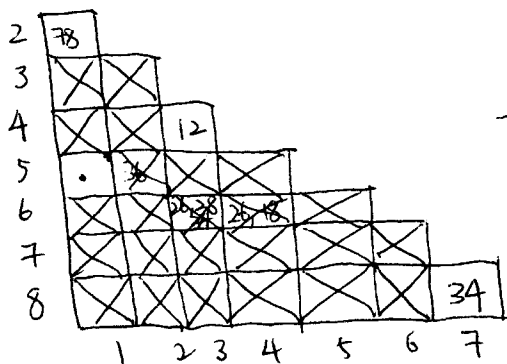

	00	01	11	10	$z_1 z_2$
$[1,2] = A$	(A)	C	D	C	00
$[1,5] = B$	A	E	D	C	00
$[3,4] = C$	E	E	A	(C)	01
$[7,8] = D$	(D)	C	B	A	10
$[6] = E$	A	(E)	D	C	01

E

From description, come up with transition table (essentially each state is the amount of carry in the circuit. A is 0 B is 1 and C is 2):

	x	
	0	1
A	A,0	B,1
B	A,1	C,0
C	B,0	C,1

Next, choose a state assignment (there are many ways of doing this),

A=00

B=01

C=11

Transition table becomes.

	x	
	0	1
00	00,0	01,1
01	00,1	11,0
11	01,0	11,1

Break up into various K-maps (assuming D Flip-flops are used for simplicity):

Y <sub>1</sub>		x	
		0	1
y <sub>1</sub> y <sub>2</sub>	00	0	0
	01	0	1
	11	0	1
	10	x	x

Y <sub>2</sub>		x	
		0	1
y <sub>1</sub> y <sub>2</sub>	00	0	1
	01	0	1
	11	1	1
	10	x	x


F		x	
		0	1
y <sub>1</sub> y <sub>2</sub>	00	0	1
	01	1	0
	11	0	1
	10	x	x

$$Y_1 = xy_2$$

$$Y_2 = x + y_1$$

$$F = xy_2' + xy_1 + x'y_1'y_2$$

Final circuit:

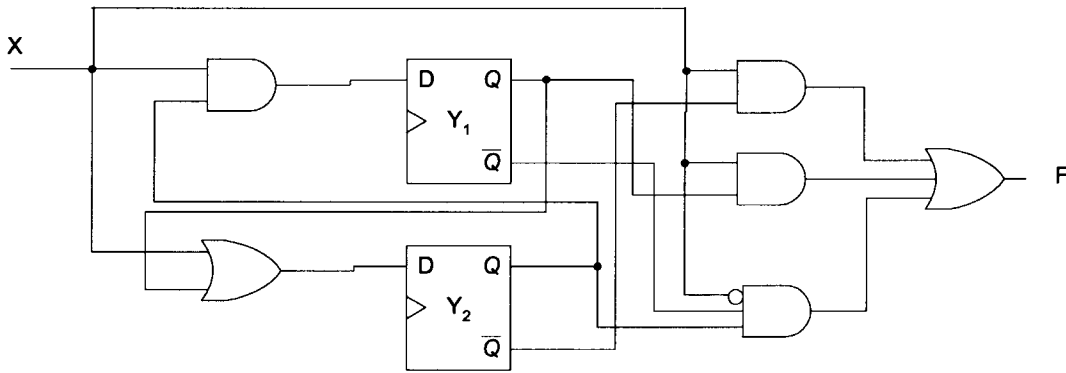

F

$$F = xy(y+z)$$

a) for b s-a-0 (same as y s-a-0)

$$f_{y=0} = 0$$

$$f_{y=1} = x$$

find solutions to:  $yx=1$

Therefore tests are  $\langle x,y,z \rangle = \langle 1,1,d \rangle$

So testability is  $2/8$ .

b) for h s-a-1

$$f = xyh \quad \text{with } h=y+z$$

$$f_{h=0} = 0$$

$$f_{h=1} = xy$$

Find solution to  $h'xy=1 = y'z'xy'=1$

No solutions exist

So testability is 0.

c) for h s-a-0

$$\text{Find solutions to } hxy = 1 = (y+z)xy = 1$$

Tests are  $\langle x,y,z \rangle = \langle 1,1,d \rangle$

so testability is  $2/8$ .