

ECE 462 Homework 3 Solutions (Spr 2005)

1. Problem 6.13(a) From Homework 2 =

$$f_1 = wxy + wx'y'z$$

$$f_2 = x'z' + wxz + xy'z$$

$$f_3 = w'z' + wxyz + w'x'y'$$

MOPI's = $wxy, w'y'z, x'z', wxz,$
 $xy'z, wxyz, w'x'y', w'x'y'z,$
 and $w'x'y'z$

	f_1				f_2						f_3						
	1	5	14	15	0	2	5	8	10	13	15	0	1	2	8	10	15
14, 15 wxy			(X)	X													
1, 5 $w'y'z$	X	X			(X)	(X)	(X)	(X)				X	(X)	(X)	(X)		
0, 2, 8, 10 $x'z'$					(X)	(X)											
13, 15 wxz									X	X							
5, 13 $xy'z$						X			X								
15 $wxyz$				X							X						(X)
0, 1 $w'x'y'$												X	X				
5 $w'xy'z$		X					X										
1 $w'x'y'z$	X																X

$$f_1 = wxy +$$

$$f_2 = x'z' +$$

$$f_3 = x'z' + wxyz$$

Eliminate columns covered by essential MOPI's

	f_1		f_2			f_3	Cg	Cd
	1	5	5	13	15	1		
1, 5 $w'y'z$	X	X					1	4
13, 15 wxz				X	X		1	4
5, 13 $xy'z$			X	X			1	4
15 $wxyz$					X		0	1
0, 1 $w'x'y'$						X	1	4
5 $w'xy'z$		X	X				1	5, 6
1 $w'x'y'z$	X					X	1	5, 6

For f_1 , (1,5) has lower cost than (5) + (1), So choose (1,5)

For f_2 , the combination with the lowest cost is (15) + (5,13)

For f_3 , (1,4) has lower cost than (1)

$$\text{So } f_1 = WxY + W'y'z$$

$$f_2 = X'z' + Xy'z + WxYz$$

$$f_3 = X'z' + WxYz + W'x'y'$$

2. Problem 6.17

Part (i) Use Quine-McCluskey Tabulation Method to determine MOP's.

	W	X	Y	Z	f_1	f_2	f_3	
0	0	0	0	0	0	1	1	✓
1	0	0	0	1	1	1	0	✓
2	0	0	1	0	0	0	1	✓
* 8	1	0	0	0	1	1	1	
3	0	0	1	1	0	0	1	✓
5	0	1	0	1	1	1	0	✓
6	0	1	1	0	0	0	1	✓
9	1	0	0	1	0	0	1	✓
10	1	0	1	0	0	0	1	✓
12	1	1	0	0	1	0	0	✓
7	0	1	1	1	1	0	0	✓
11	1	0	1	1	0	0	1	✓
13	1	1	0	1	1	0	0	✓
* 14	1	1	1	0	1	1	1	
15	1	1	1	1	1	0	0	✓

⇒
next Page

2 Continued:

	W	X	Y	Z	f ₁	f ₂	f ₃
* (0,1)	0	0	0	-	0	1	0
(0,2)	0	0	-	0	0	0	1 ✓
* (0,8)	-	0	0	0	0	1	1
* (1,5)	0	-	0	1	1	1	0
(2,3)	0	0	1	-	0	0	1 ✓
(2,6)	0	-	1	0	0	0	1 ✓
(2,10)	-	0	1	0	0	0	1 ✓
(8,9)	1	0	0	-	0	0	1 ✓
(8,10)	1	0	-	0	0	0	1 ✓
* (8,12)	1	-	0	0	1	0	0
(3,11)	-	0	1	1	0	0	1 ✓
(5,7)	0	1	-	1	1	0	0 ✓
(5,13)	-	1	0	1	1	0	0 ✓
(6,14)	-	1	1	0	0	0	1 ✓
(9,11)	1	0	-	1	0	0	1 ✓
(10,11)	1	0	1	-	0	0	1 ✓
(10,14)	1	-	1	0	0	0	1 ✓
(12,13)	1	1	0	-	1	0	0 ✓
(12,14)	1	1	-	0	1	0	0 ✓
(7,12)	-	1	1	1	1	0	0 ✓
(13,15)	1	1	-	1	1	0	0 ✓✓
(14,15)	1	1	1	-	1	0	0 ✓✓

⇒

2 continued:

	W	X	Y	Z	f ₁	f ₂	f ₃
* (0, 8, 2, 10)	-	0	-	0	0	0	1
* (2, 10, 3, 11)	-	0	1	-	0	0	1
* (2, 10, 6, 14)	-	-	1	0	0	0	1
* (8, 9, 10, 11)	1	0	-	-	0	0	1
* (5, 13, 7, 15)	-	1	-	1	1	0	0
* (12, 14, 13, 15)	1	1	-	-	1	0	0

So map1's are: For f₁, f₂, f₃ = $wx'y'z$, $wxyz'$
 For f₂, f₃ = $x'y'z'$ For f₁, f₂ = $w'y'z$
 For f₁ = $wy'z'$, xz , wx
 For f₂ = $w'x'y'$
 For f₃ = $x'z'$, $x'y$, yz' , wx'

Part (ii)

	f ₁					f ₂					f ₃											
	1	5	7	8	12	13	14	15	0	1	5	8	14	0	2	3	6	8	9	10	11	14
8 $wx'y'z$				x								x							x			
14 $wxyz'$							x						⊗									x
0, 8 $x'y'z'$									x		x			x					x			
1, 5 $w'y'z$	⊗	x									x	⊗										
8, 12 $wy'z'$				x	x																	
5, 7, 13, 15 xz		x	⊗			x		x														
12, 13, 14, 15 wx					x	x	x	x														
0, 1 $w'x'y'$									x	x												
0, 2, 8, 10 $x'z'$														x	x			x		x		
2, 3, 10, 11 $x'y$														x	⊗				x	x		
2, 6, 10, 14 yz'														x	⊗				x			x
8, 9, 10, 11 wx'																		x	⊗	x	x	

So $f_1 = w'y'z + xz +$

$f_2 = wxyz' + w'y'z +$

$f_3 = x'y + yz' + wx' +$

Eliminate the columns covered by essential mops to get

	f1			f2		f3	Cg	Cd
	8	12	14	0	8	0		
8 $wx'y'z$	X				X		1	5,6
14 $wxyz'$			X				0	1
0,8 $x'y'z'$				X	X	X	1	4,5
8,12 $wy'z'$	X	X					1	4
12,13,14,15 wx		X	X				1	3
0,1 $w'x'y'$				X			1	4
0,2,8,10 $x'z'$						X	1	3

For f_1 , the combination for the lowest cost is (14) + (8, 12)

For f_2 , (0,8) has lower cost than (8) + (0,1)

For f_3 , since (0,8) is chosen for f_2 , the gate cost for (0,8) becomes 0. So choose (0,8) over (0,2,8,10).

Therefore,

$$f_1 = w'y'z + xz + wxyz' + wy'z'$$

$$f_2 = wxyz' + w'y'z + x'y'z'$$

$$f_3 = x'y + yz' + wx' + x'y'z'$$

3. Problem 5.6 (a)

$$S_{1,3,5,7}(x_1, \dots, x_7) S_{4,5,6,7}(x_1, \dots, x_7) = S_{5,7}(x_1, \dots, x_7)$$

Reason: When ANDing two symmetric functions, only the S_a terms that appear in both functions will remain. To illustrate this, consider the following (smaller) example:

$$S_{1,2}(a,b,c) S_{2,3}(a,b,c).$$

Expand these out into regular functions:

$$(ab'c' + a'bc' + a'b'c + abc' + ab'c + a'bc)(abc' + ab'c + a'bc + abc)$$

Each term in the left portion, when multiplied out will cancel with every term in the right half, except if it is identical. For example $ab'c' * abc' = abb'c' = 0$. Therefore after this is multiplied out, only the following terms remain: $abc' + ab'c + a'bc = S_2(a,b,c)$

This works in general as well under similar logic.

Problem 5.6 (d)

$$x_1' S_{0,1,2}(x_2, x_3, x_4) + x_1 S_{2,3}(x_2', x_3', x_4') = S_{0,1,2}(x_1, x_2, x_3, x_4)$$

To arrive at this, first express $S_{2,3}(x_2', x_3', x_4')$ as a function of only x_2, x_3, x_4 :

$$S_{2,3}(x_2', x_3', x_4') = S_{0,1}(x_2, x_3, x_4).$$

To see this, consider, only the $S_3(x_2', x_3', x_4')$ term. This will be 1 when each of its variables are 1, i.e. $x_2 = x_3 = x_4 = 0$. This is the same as $S_0(x_2, x_3, x_4)$.

Now the following changes can be made (expand them out if you don't understand the reasoning).

$$x_1' S_0(x_2, x_3, x_4) = S_0(x_1, x_2, x_3, x_4)$$

$$x_1 S_0(x_2, x_3, x_4) + x_1' S_1(x_2, x_3, x_4) = S_1(x_1, x_2, x_3, x_4)$$

$$x_1 S_1(x_2, x_3, x_4) + x_1' S_2(x_2, x_3, x_4) = S_2(x_1, x_2, x_3, x_4)$$

4. Problem 5.7 (e)

K-Map:

		WX			
		00	01	11	10
yz	00	1	1	0	1
	01	1	1	0	1
	11	1	0	0	0
	10	1	0	0	0

$$F(w,x,y,z) = w'x' + w'y' + x'y'$$

W:

$$fw : x'y'$$

$$fw' : x'+y'+x'y'$$

$fw \Rightarrow fw'$ negative in w

X:

$$fx : w'y'$$

$$fx' : w'+w'y'+y'$$

$fx \Rightarrow fx'$ negative in x

Y:

$$fy : w'x'$$

$$fy' : w'x'+w'+x'$$

$fy \Rightarrow fy'$ negative in y

Z:

$$fz : w'x'+w'y'+x'y'$$

$$fz' : w'x'+w'y'+x'y'$$

$fz = fz'$ vacuous in z

Therefore it is unate, since it is negative in w,x,y and vacuous in z (which is trivially positive or negative)

Problem 5.7 (f) K-Map:

		WX			
		00	01	11	10
yz	00	1	1	0	0
	01	1	1	0	0
	11	1	0	0	0
	10	1	0	0	0

$$F(w,x,y,z)=w'x'+w'y'$$

W:

$$fw : 0$$

$$fw' : x'+y'$$

$fw \Rightarrow fw'$ negative in w

X:

$$fx : w'y'$$

$$fx' : w'+w'y'$$

$fx \Rightarrow fx'$ negative in x

Y:

$$fy : w'x'$$

$$fy' : w'x'+w'$$

$fy \Rightarrow fy'$ negative in y

Z:

$$fz: w'x' + w'y'$$

$$fz': w'x' + w'y'$$

$$fz = fz' \text{ vacuous in } z$$

Therefore it is unate (same reason as in previous problem).

5.

$f_{xi} * f_{xi}' = f_{xi}'$ means that whenever f_{xi}' is 1, $f_{xi} * f_{xi}'$ is also 1, and therefore f_{xi} is also 1. By definition then $f_{xi} \Rightarrow f_{xi}'$ (see Page 171 on text book). Thus by theorem 5.3-3 (Page 172 on text book) f is positive in xi .

6.

w	x	y	z	f
0	0	0	0	0 $0 < T$
0	0	0	1	0 $a_z < T$
0	0	1	0	0 $a_y < T$
0	0	1	1	0 $a_y + a_z < T$
0	1	0	0	0 $a_x < T$
0	1	0	1	0 $a_x + a_z < T$
0	1	1	0	0 $a_x + a_y < T$
0	1	1	1	0 $a_x + a_y + a_z < T$
1	0	0	0	0 $a_w < T$
1	0	0	1	0 $a_w + a_z < T$
1	0	1	0	0 $a_w + a_y < T$
1	0	1	1	1 $a_w + a_y + a_z > T$
1	1	0	0	1 $a_w + a_x > T$
1	1	0	1	1 $a_w + a_x + a_z > T$
1	1	1	0	1 $a_w + a_x + a_y > T$
1	1	1	1	1 $a_w + a_x + a_y + a_z > T$

One possible solution to satisfy all of these:

$$a_w = 5$$

$$a_x = 2$$

$$a_y = 1$$

$$a_z = 1$$

$$T = 6.5$$

7. Prove $f = (x' + y')(x + wy)$ is not a threshold function in two methods:

Method 1: prove threshold does not exist:

W	X	Y	f		
0	0	0	0		
0	0	1	0		
0	1	0	1	$a_x > T$	(A)
0	1	1	0	$a_x + a_y < T$	(B)
1	0	0	0	$a_w < T$	(C)
1	0	1	1	$a_w + a_y > T$	(D)
1	1	0	1		
1	1	1	0		

From condition (A) and (B), $a_y < 0$ (E)
 (C) + (E) $\Rightarrow a_w + a_y < T$ **contradicts** (D)
 Hence the threshold does not exist.

Method 2: Prove the function is not unate.

$$f_x = f(w, x=1, y) = y'$$

$$f_x' = f(w, x=0, y) = wy$$

$f_x * f_x' = 0 \neq f_x$ or f_x' . f_x and f_x' are not compatible; f is mixed in x .
 Hence f is not unate, and therefore not a threshold function.