


# ECE 462 Homework 5 Solutions

1. From Homework 5, the static-0 hazards exist for transitions

$ABCD: \langle 1001 \rangle \leftarrow \langle 1011 \rangle$   
 $\langle 1110 \rangle \leftarrow \langle 1010 \rangle$   
 $\langle 1000 \rangle \leftarrow \langle 1010 \rangle$


plot the timing diagrams as following:

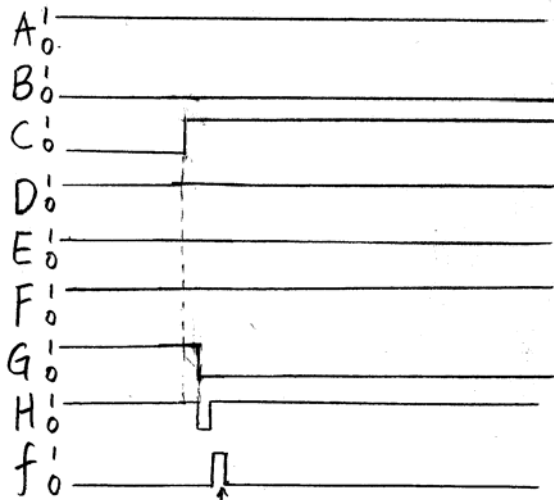$ABCD \langle 1001 \rangle \leftarrow \langle 1011 \rangle$





↑ static-zero hazard

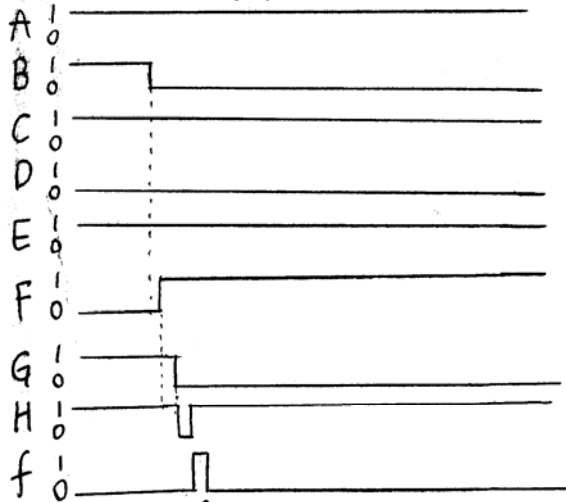$ABCD \langle 1110 \rangle \leftarrow \langle 1010 \rangle$



↑ static-zero hazard

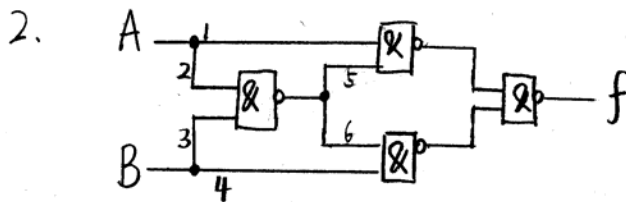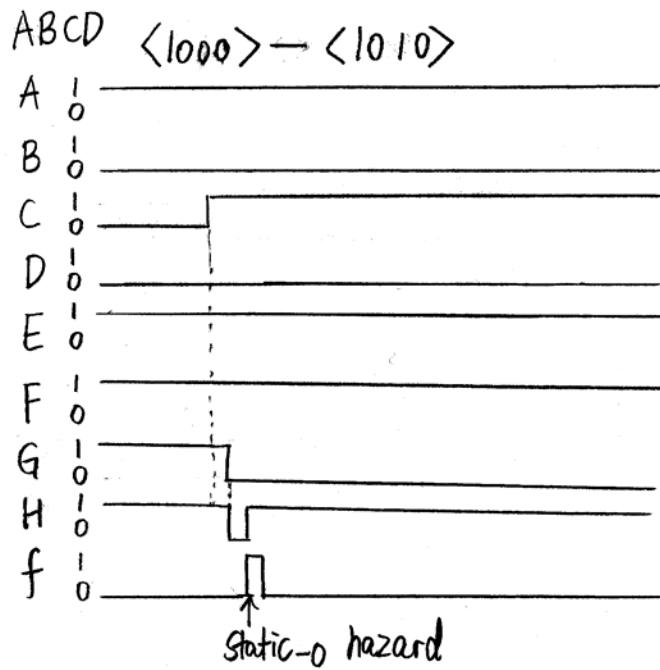

(i)  $f(A, B) = [ (A_1 (A_{3,5} B_{3,5})')' (B_4 (A_{2,6} B_{3,6})')' ]'$   
 (Let  $A_{2,5} = A_7, A_{2,6} = A_8, B_{3,5} = B_7, B_{3,6} = B_8$ )

$$= (A_1 (A_7 B_7)') + (B_4 (A_8 B_8)')$$

$$= A_1 (A_7' + B_7') + B_4 (A_8' + B_8')$$

$$= A_1 A_7' + A_1 B_7' + A_8' B_4 + B_4 B_8'$$

P-sets =  $[A_1, A_7'], [A_1, B_7'], [A_8', B_4], [B_4, B_8']$

$$f = A_1 (A_7' + B_7') + B_4 (A_8' + B_8')$$

$$f^D = (A_1 + A_1' B_7') (B_4 + A_8' B_8')$$

Continue  $f^D$ :

$$= A_1 B_4 + A_1 A_8' B_8' + A_7' B_7' B_4 + A_7' A_8' B_7' B_8'$$

$$f = (f^D)^D = (A_1 + B_4) (A_1 + A_8' + B_8') (A_7' + B_7' + B_4) (A_7' + A_8' + B_7' + B_8')$$

$$S\text{-sets} = [A_1, B_4], [A_1, A_8', B_8'], [A_7', B_7', B_4], [A_7', A_8', B_7', B_8']$$

(ii) Unstable P-sets =  $[A_1, A_7'] [B_4, B_8']$

Stable P-sets =  $[A_1, B_7'] [A_8', B_4]$

1) Let  $U_1 = [A_1, A_7']$ ,  $X_1 = A \{1, 7\}$

2) Let  $B_1 = [A_8', B_4]$

3)  $B=1$

4) No work

Use the steps corresponding to the procedures listed on Page 91

⇒ **Dynamic hazard  $\langle A, B \rangle = \langle 0, 1 \rangle - \langle 1, 1 \rangle$  (A changing,  $B=1$ )**

1) Let  $U_2 = [B_4, B_8']$ ,  $X_2 = B \{4, 8\}$

2) Let  $B_2 = [A_1, B_7']$

3)  $A=1$

4) No work

⇒ **Dynamic hazard  $\langle A, B \rangle = \langle 1, 0 \rangle - \langle 1, 1 \rangle$  ( $A=1$ , B changing)**

(iii) Unstable S-sets =  $[A_1, A_8', B_8']$ ,  $[A_7', B_7', B_4]$

Stable S-sets =  $[A_1, B_4]$ ,  $[A_7', A_8', B_7', B_8']$

1) Let  $U_1 = [A_1, A_8', B_8']$ ,  $X_1 = A \{1, 8\}$

2) Let  $B_1 = [A_7', A_8', B_7', B_8']$

3)  $B=1$

4) No work

⇒ **Dynamic hazard  $\langle A, B \rangle = \langle 0, 1 \rangle - \langle 1, 1 \rangle$  (A changing,  $B=1$ )**

Page 3

1) Let  $u_2 = [A_1', B_1', B_4]$ ,  $x_2 = B\{7, 4\}$

2) Let  $B_2 = [A_1', A_8', B_1', B_8']$


3)  $A=1$

4) No work


⇒ **Dynamic hazard:  $\langle A, B \rangle = \langle 10 \rangle - \langle 11 \rangle$  (or  $A=1$ ,  $B$  changing)**

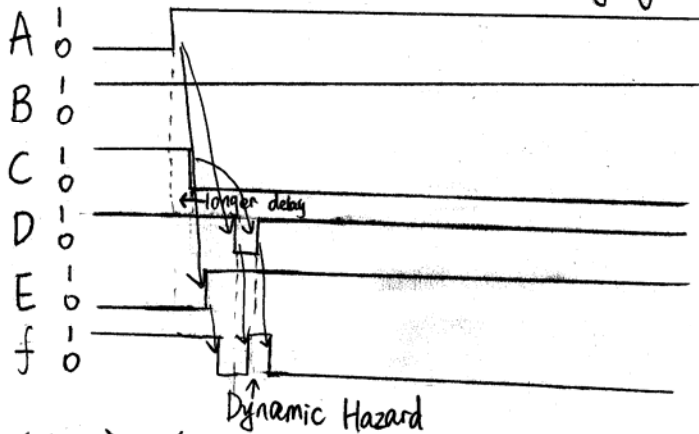3. Plot the two dynamic hazards discovered in Problem 2:

$\langle A, B \rangle = \langle 01 \rangle - \langle 11 \rangle$  (or  $A$ -changing,  $B=1$ )




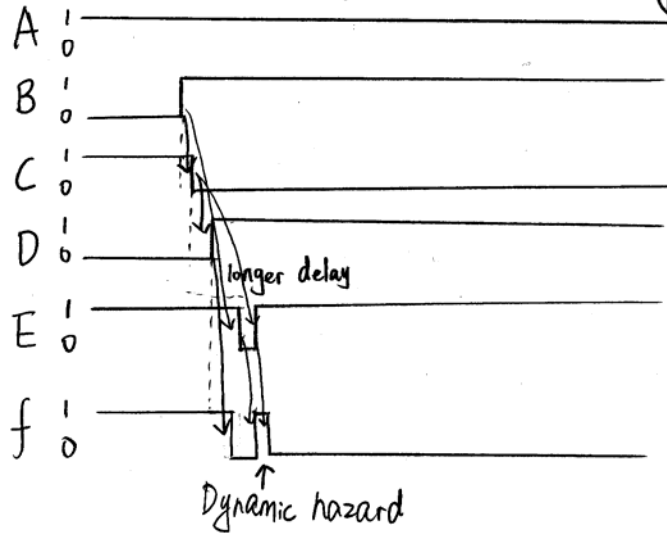$\langle A, B \rangle = \langle 10 \rangle - \langle 11 \rangle$  ( $A=1$ ,  $B$  changing)



4. Problem 3.9

Mark the Logic Diagram as following:

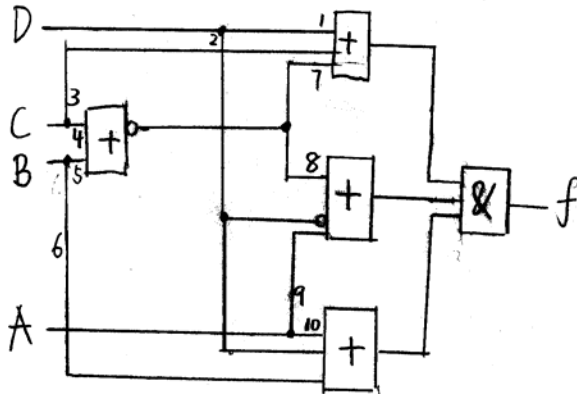

$$(a) f = (D_1 + C_3 + (C_4 + B_5)'_7) ((C_4 + B_5)'_8 + D_2' + A_9) (A_{10} + D_2 + B_6)$$

$$f^D = D_1 C_3 (C_{4,7} B_{5,7})' + (C_{4,8} B_{5,8})' D_2' A_9 + A_{10} D_2 B_6$$

(Let  $C_{4,7} = C_{11}, C_{4,8} = C_{12}, B_{5,7} = B_{11}, B_{5,8} = B_{12}$ )

$$= D_1 C_3 (C_{11}' + B_{11}') + (C_{12}' + B_{12}') D_2' A_9 + A_{10} D_2 B_6$$

$$= D_1 C_3 C_{11}' + D_1 C_3 B_{11}' + C_{12}' D_2' A_9 + B_{12}' D_2' A_9 + A_{10} D_2 B_6$$

$$f = f^{PD} = (D_1 + C_3 + C_{11}') (D_1 + C_3 + B_{11}') (C_{12}' + D_2' + A_9) (B_{12}' + D_2' + A_9) (A_{10} + D_2 + B_6)$$

So the S-sets:  $[D_1, C_3, C_{11}'], [D_1, C_3, B_{11}'], [C_{12}', D_2', A_9], [B_{12}', D_2', A_9], [A_{10}, D_2, B_6]$

(b)

		CD			
		00	01	11	10
AB	00	0	1	0	0
	01	0	0	0	1
	11	0	1	1	1
	10	1	1	1	1

k-Map with S-sets

Continue 4

(c)

$$U = [D_1, C_3, C_{11}'] , X = C$$

$$B = [C_{12}', P_2', A_9]$$

In order to make U active,  $D = 0$

In order to make B active,  $D = 1, A = 0$  > conflicts with each other

Hence it is impossible to make U and B active at the same time

There are no other possible combination of U and B.

Therefore, no dynamic hazard exists.

5. The K-Map of the logic circuit is as following:

		00	01	11	10
AB	00	0 <sub>0</sub>	0 <sub>1</sub>	1 <sub>3</sub>	1 <sub>2</sub>
	01	0 <sub>4</sub>	1 <sub>5</sub>	1 <sub>6</sub>	1 <sub>7</sub>
	11	0 <sub>8</sub>	1 <sub>9</sub>	1 <sub>10</sub>	0 <sub>11</sub>
	10	0 <sub>12</sub>	0 <sub>13</sub>	0 <sub>14</sub>	0 <sub>15</sub>

The prime implicants are  $BD$  (5,7,13,15) and  $\bar{A}C$  (2,3,6,7)  
 Use the tabular method to determine hazard-free minimal sum

	(2,3)	(2,6)	(3,7)	(5,7)	(6,7)	(5,13)	(7,15)	(13,15)
$BD(5,7,13,15)$				X		X	X	X
$\bar{A}C(2,3,6,7)$	X	X	X		X			

The table shows that all the 1 pairs are covered by the prime implicants.  
 Hence the hazard-free minimal sum is:

$$f = BD + \bar{A}C$$