

Homework 9 Solutions

(A) Put amplifiers at the feedback loops of Q_1 and Q_2 and call the signals y_1 and y_2 .

Excitation Functions:

$$S_1 = X_2 y_2, R_1 = X_1 y_2, S_2 = X_2 \bar{y}_1 + X_1 y_1, R_2 = X_1 + X_2$$

So the transition table is

		$X_1 X_2$			
		00	01	11	10
$y_1 y_2$	00	00	01	01	00
	01	01	11	11	00
	11	11	10	11	01
	10	10	10	11	11
		$Y_1 Y_2$			

→ state table

		$X_1 X_2$			
		00	01	11	10
S_1	1	1	2	2	1
	2	2	3	3	1
	3	3	4	3	2
	4	4	4	3	3
		S			

So the flow table is

		$X_1 X_2$			
		00	01	11	10
S	1	1	4	3	1
	2	2	4	3	1
	3	3	4	3	1
	4	4	4	3	1
		S			

(B) One such flow table that contains an essential hazard is :

$S_2R \quad (S_1=0)$

S	00	01	11	10
1	①	1	①	2
2	②	1	1	②
3	③	4	4	③
4	④	④	④	3
5	⑤	4	4	3

$S_2R \quad (S_1=1)$

S	00	01	11	10
1	①	①	①	①
2	②	3	3	②
3	③	③	③	③
4	④	1	1	④
5	⑤	⑤	⑤	⑤

In this flow-table, an essential hazard exists when and internal state 3,

$S_2=0, R=1$, and S_1 changes from 0 to 1.

If S_1 changes from 0 to 1 once, it ends up in state

3. If S_1 changes two more times, the machine ends up in state 4 which is different than 3.

Hence it is an essential hazard.

(C)

Excitation equations:

$$\begin{aligned}
 J_1 &= XQ_2 \\
 K_1 &= X'Q_2' \\
 J_2 &= X'Q_1 \\
 K_2 &= XQ_1' \\
 Z &= XQ_1'
 \end{aligned}$$

Transition table:

Q1Q2	X	
	0	1
00	00	00
01	01	10
11	11	11
10	01	10


Q1+Q2+

State/Output table:

s	X	
	0	1
A 00	A,0	A,1
B 01	B,0	D,1
C 11	C,0	C,0
D 10	B,0	D,0

S

State/Output diagram:

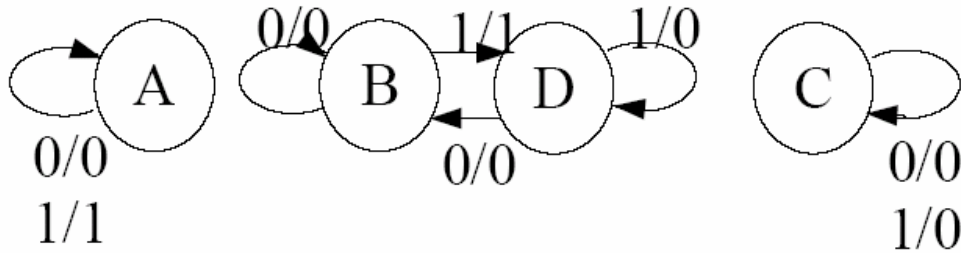

(D)

Partitioning according to their outputs we get the following grouping:

- 0110 – [1, 3, 4]
- 1011 – [2, 6, 7, 8]
- 1100 – [5]

Looking at the next state, we see that 8 is distinguishable from [2, 6, 7] when $X_1X_2 = 10$. Now we see that 7 is distinguishable from [2, 6] when $X_1X_2 = 01$. So we form the indistinguishability classes:

- [1, 3, 4] – A
- [2, 6] – B
- [5] – C
- [7] – D
- [8] – E

Reduced state table:

s	X1X2			
	00	01	11	10
A	B,0	C,1	A,1	A,0
B	A,1	E,0	A,1	C,1
C	B,1	C,1	A,0	D,0
D	A,1	B,0	A,1	C,1
E	A,1	B,0	A,1	A,1

S, Z

(E) Based on the flow table, the transition table should be:

		$X_1 X_2$			
		00	01	11	10
$y_1 y_2$	00	01	11	10	11
	01	11	10	00	10
	11	10	00	01	00
	10	00	01	11	01

⇒

		$X_1 X_2$								
		00	01	11	10					
$y_1 y_2$	00	0	1	1	1	00	d	d	d	d
	01	1	1	0	1	01	d	d	d	d
	11	d	d	d	d	11	0	1	1	1
	10	d	d	d	d	10	1	1	0	1

		$X_1 X_2$								
		00	01	11	10					
$y_1 y_2$	00	1	1	0	1	00	d	d	d	d
	01	d	d	d	d	01	0	1	1	1
	11	d	d	d	d	11	1	1	0	1
	10	0	1	1	1	10	d	d	d	d

So $J_1 = X_1 \bar{X}_2 + X_2 \bar{y}_2 + y_2 \bar{X}_1$, $K_1 = \bar{y}_2 \bar{X}_1 + y_2 X_2 + X_1 \bar{X}_2$
 $J_2 = \bar{y}_1 \bar{X}_1 + y_1 X_2 + X_1 \bar{X}_2$, $K_2 = \bar{y}_1 X_2 + y_1 \bar{X}_1 + X_1 \bar{X}_2$

So the implementation of this machine with J-k flip-flop is :

